 



Bias generator tutorial

Tobi Delbruck
ETH/Univ Zurich

Andre van Schaik
Univ. of Sydney




Chip with bias generator

 

What we will discuss


- When and why you need a bias generator
- Why bias *currents* and not bias *voltages* are important
- How to make a master reference current
- How to ensure it starts up correctly
- How to split the master by octaves
- How to make specific individual bias currents from the splitter
- How to use the bias generator design kit to compile final layout from a schematic specification

 Neuromorphic chips often use a very wide range of dynamics (6+ decades), spanning μA to pA ($\text{V}/\mu\text{s}$ to V/s). Historically, the required bias currents in experimental chips have been specified by schemes like these:



These methods are NOT manufacturable. Each chip needs custom adjustment. The currents vary with supply voltage. You don't know that your chip can actually be built in quantity. Users are hard to support. **BAD!**

Why bias currents and not bias voltages?

 


$$g_m = \frac{dI}{dV_g} \propto \frac{I}{U_T}$$

$$I = I_0 e^{kV_g}$$


$$I_0 \propto e^{-V_T}$$

Mismatched
threshold
voltage


The basic idea

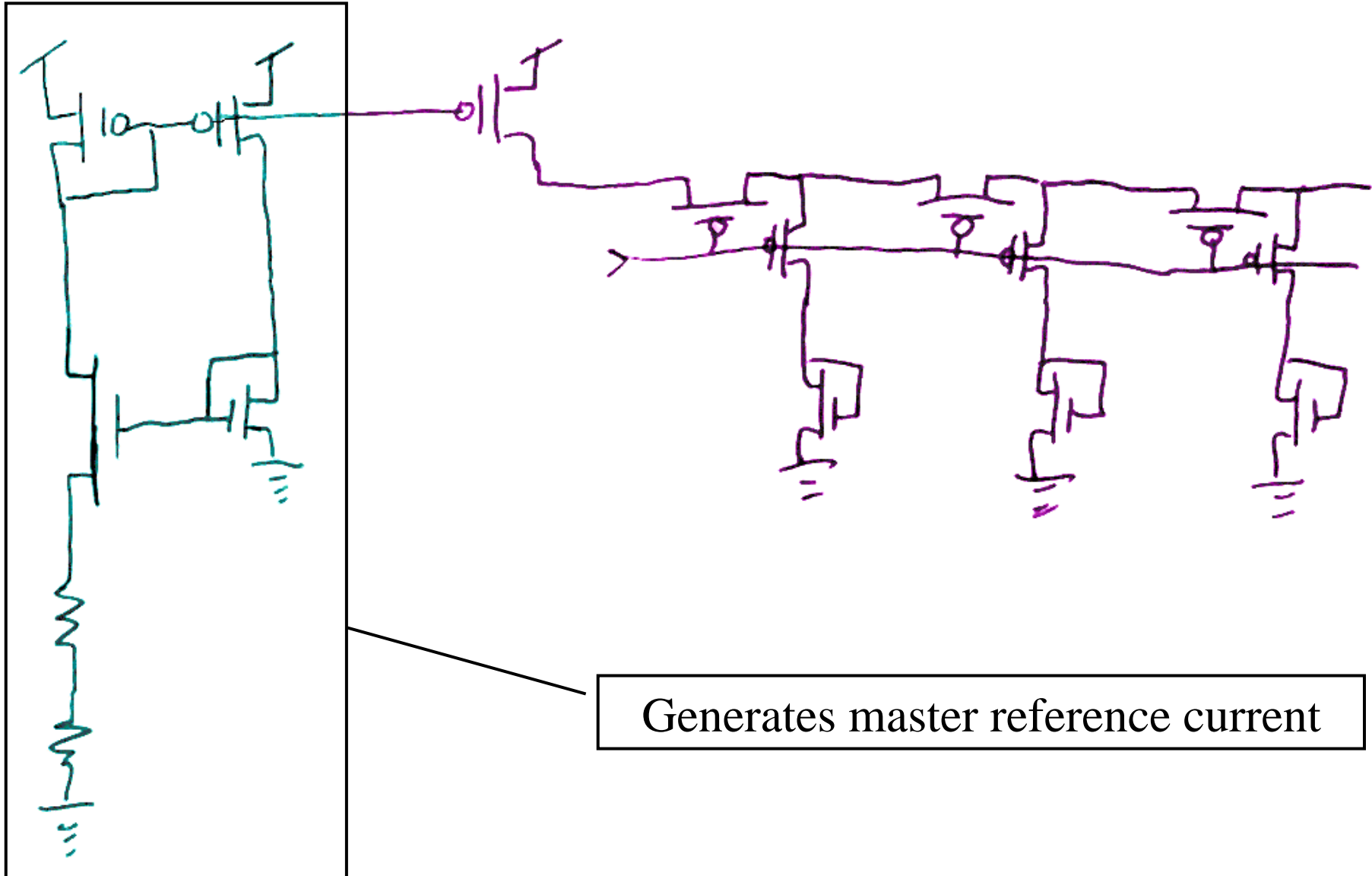


The basic idea

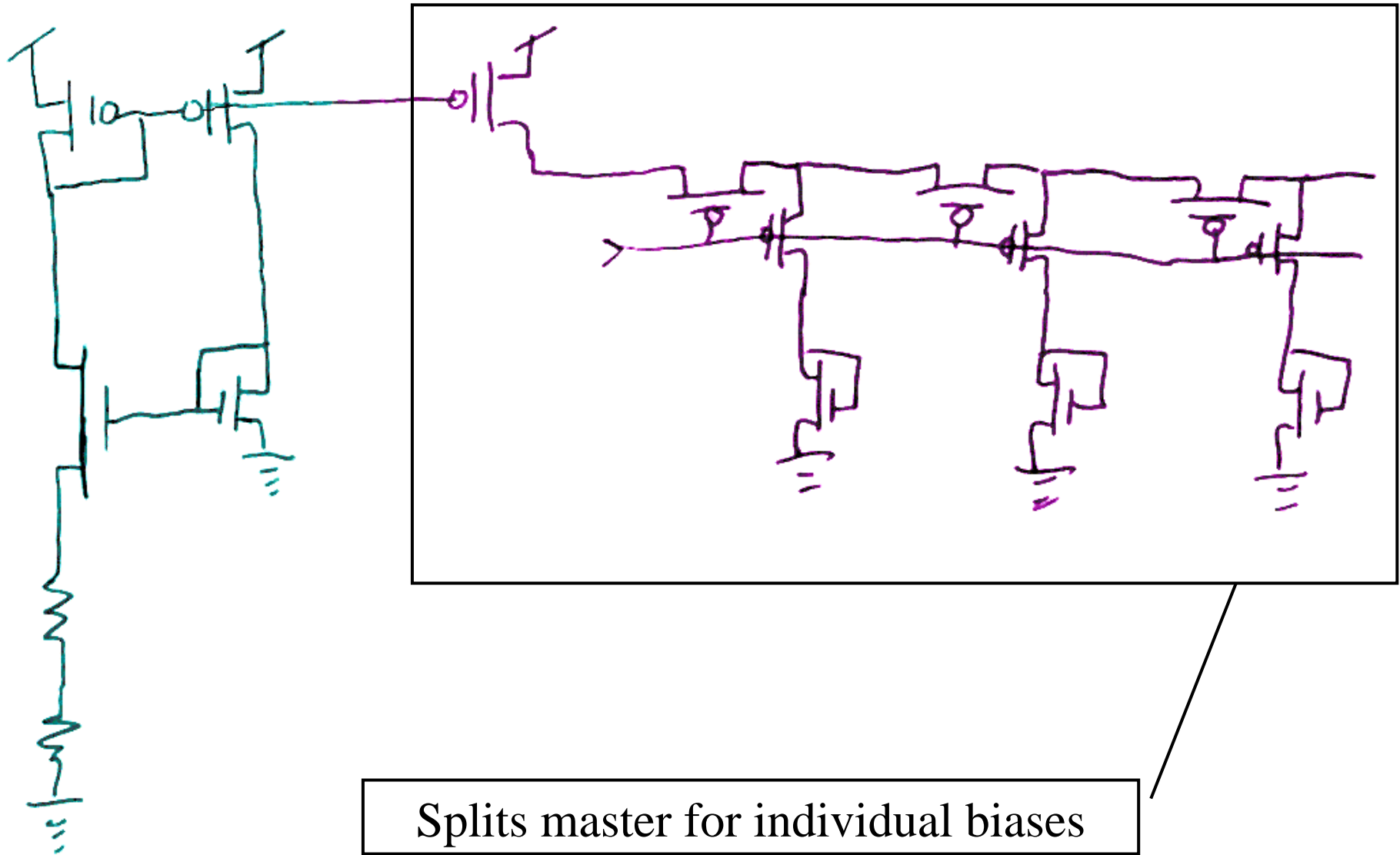


Bias generator core circuit

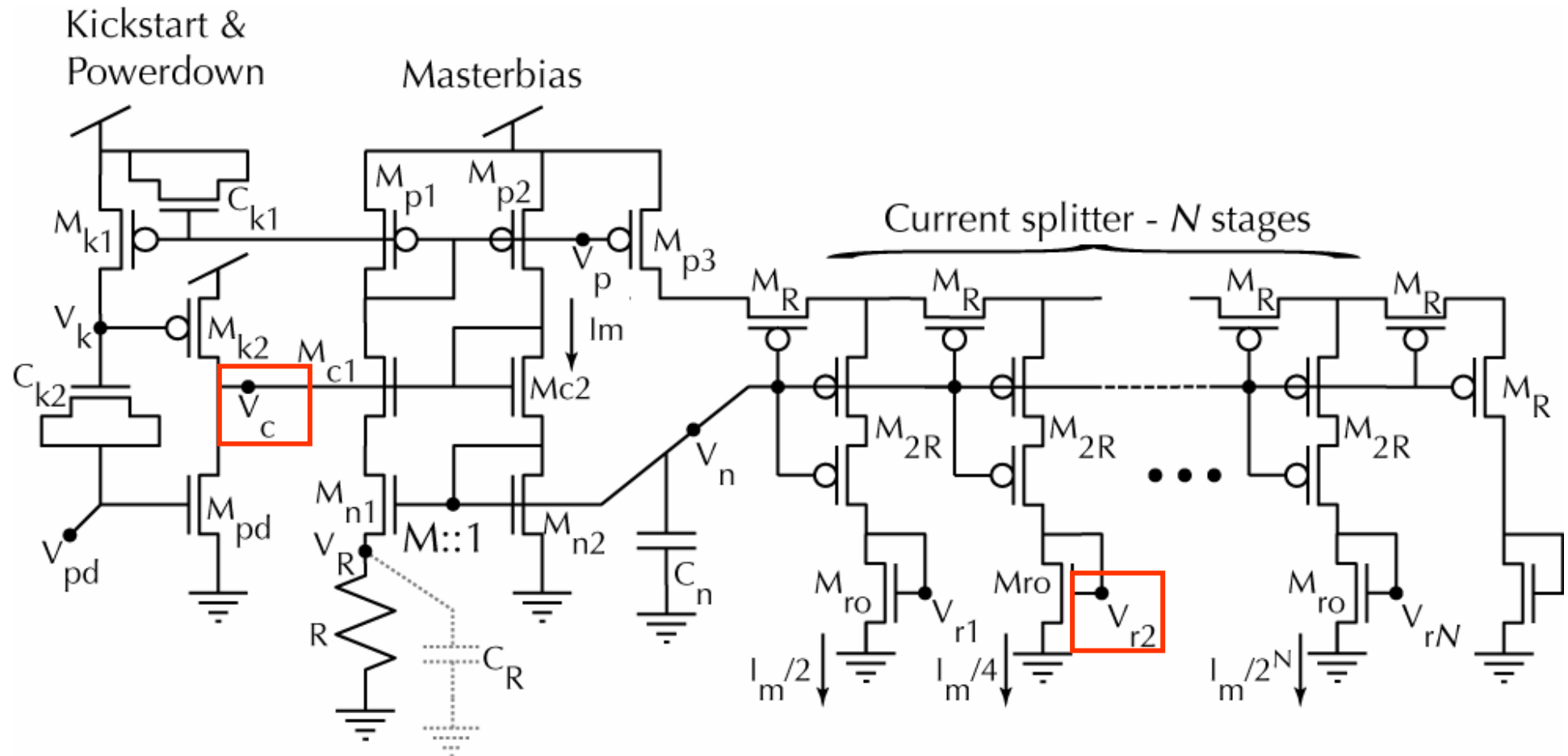

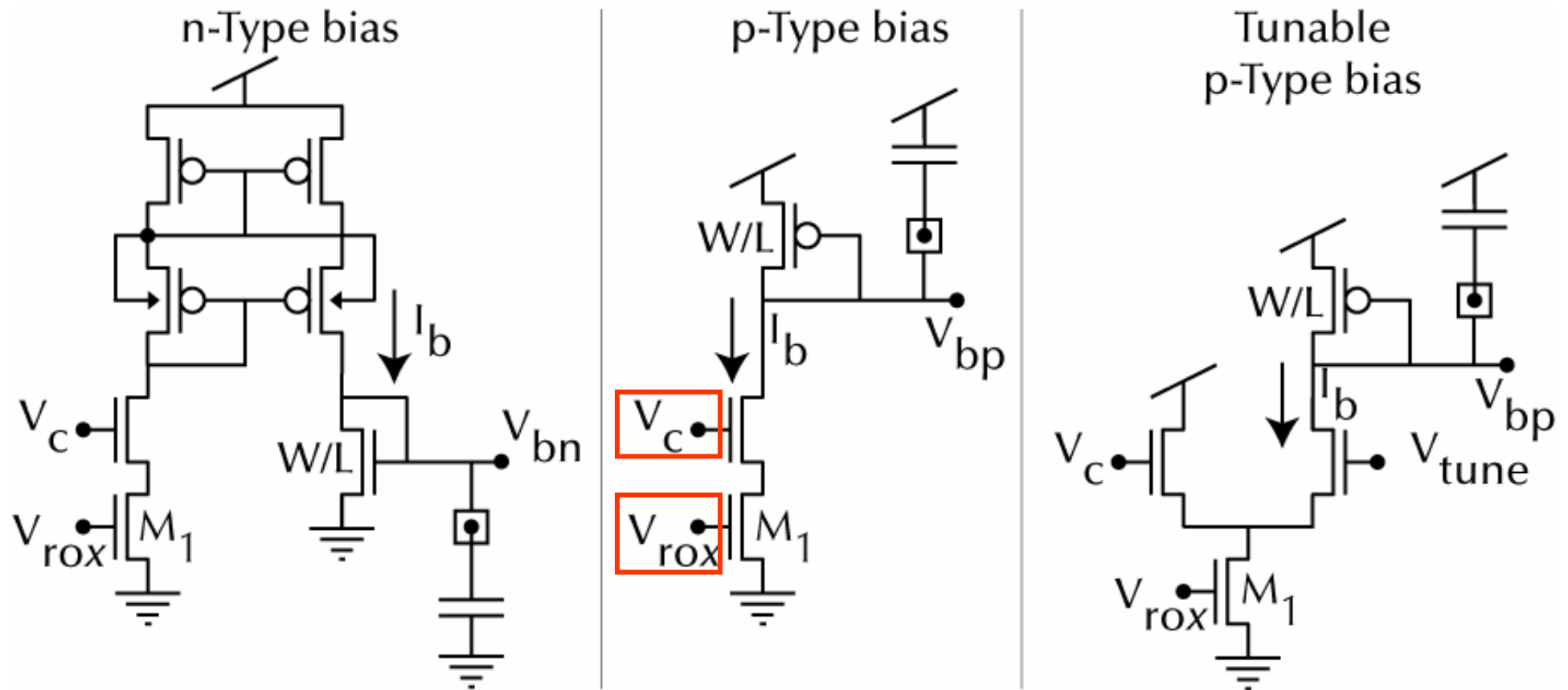Individual biases are created from the splitter currents



Bias generator core circuit

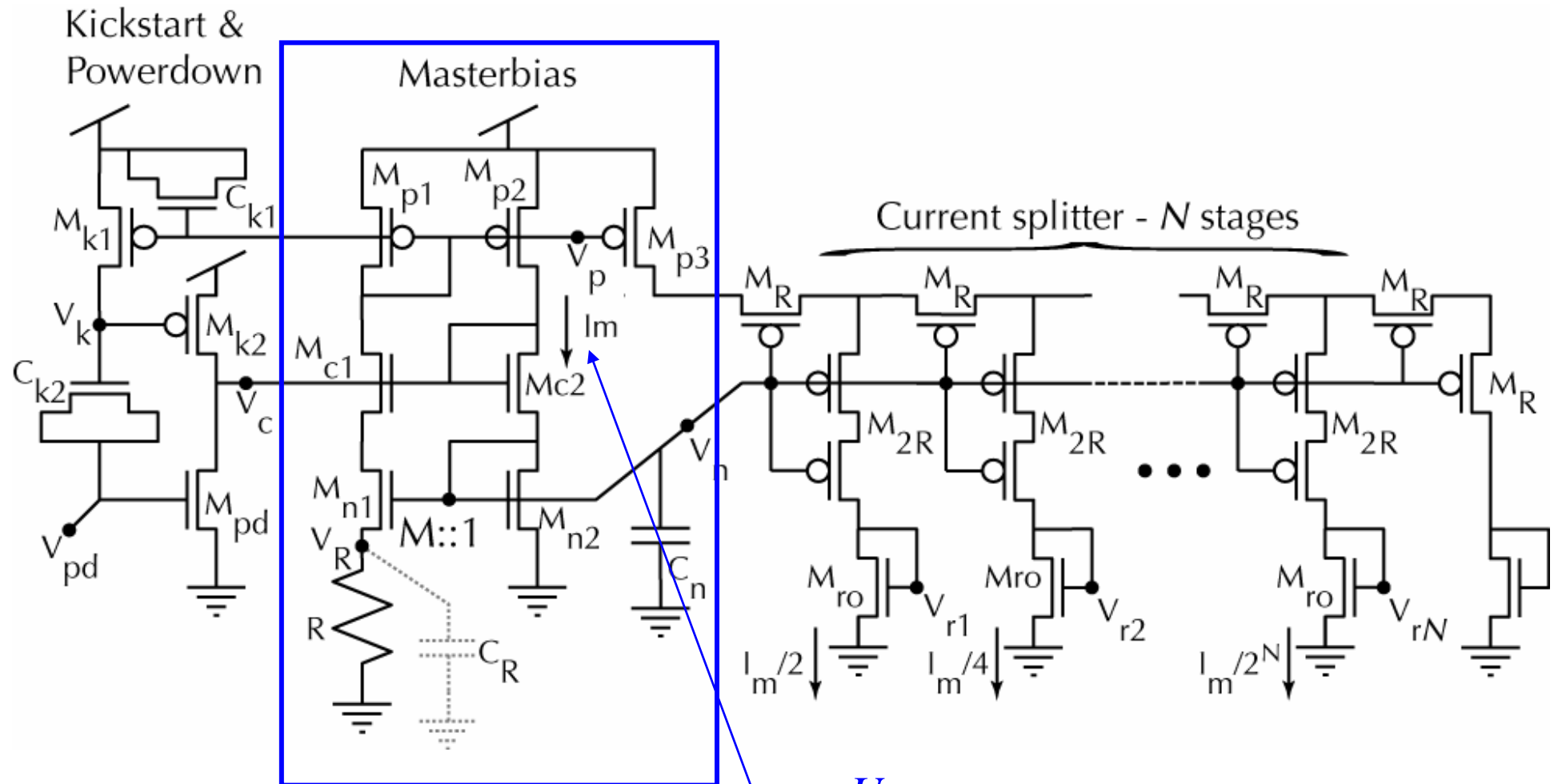



$$I_m = \frac{U_T}{R} \log(M)$$

Historical development of masterbias

- Bob Widlar,
1960's?,
bipolar
bootstrapped
current
reference

1977, LM10 opamp

 


 

One big gotcha


The masterbias
will oscillate if
 $C_r \approx C_n$

Keep C_r much
smaller than C_n

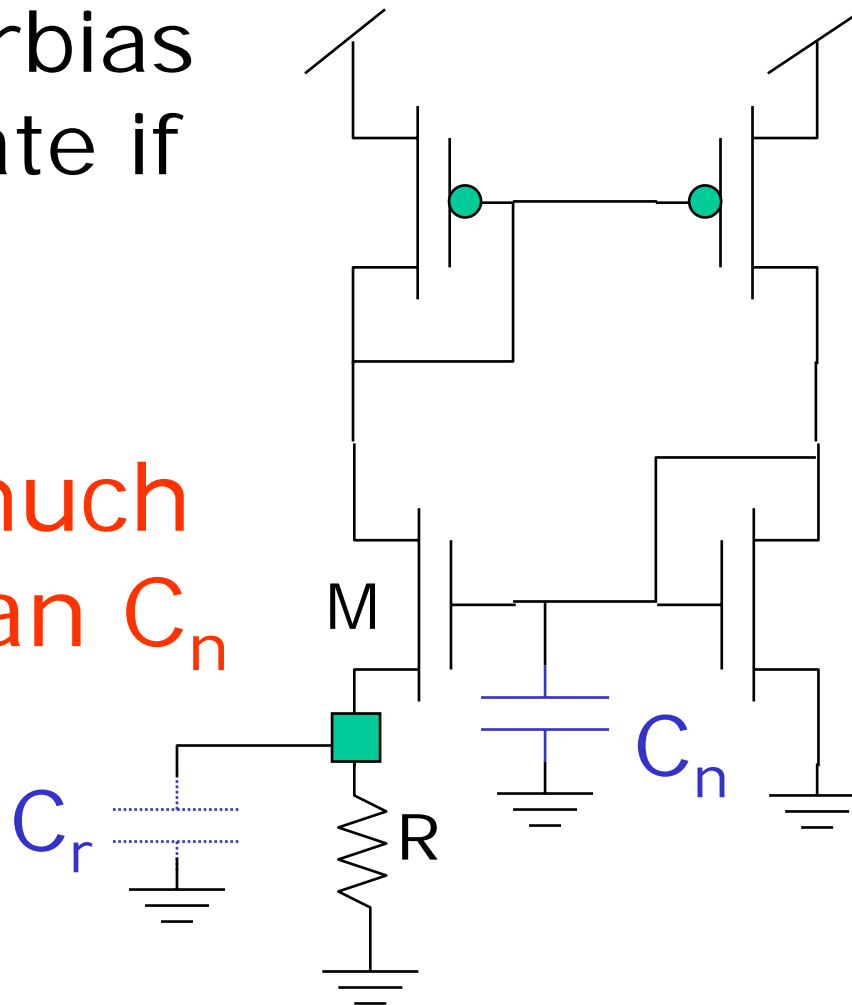



Kickstart and soft power control

$I = 0$ is also
a stable operating
point

 


Bias generator core circuit

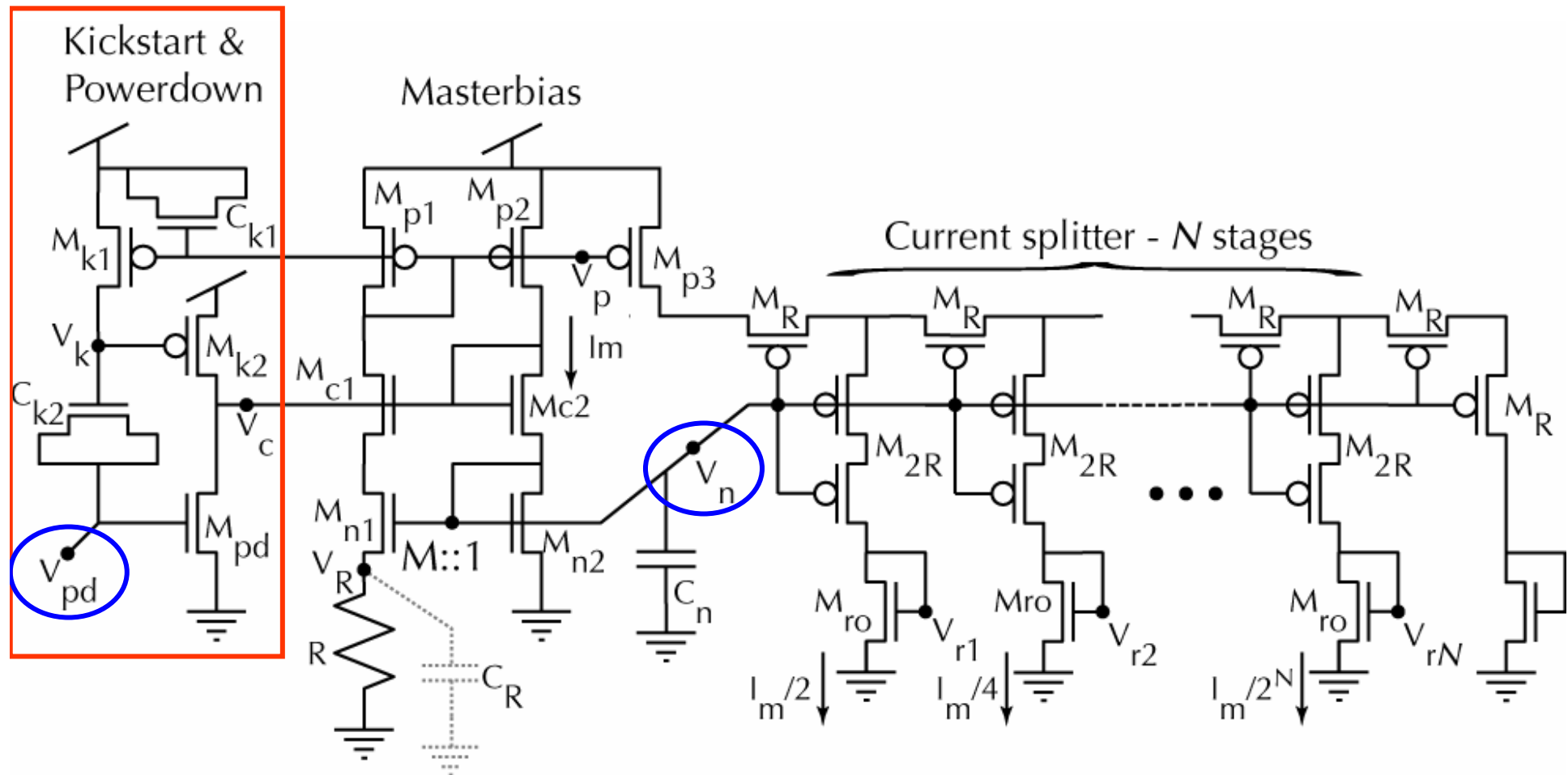

 

Bias generator core circuit

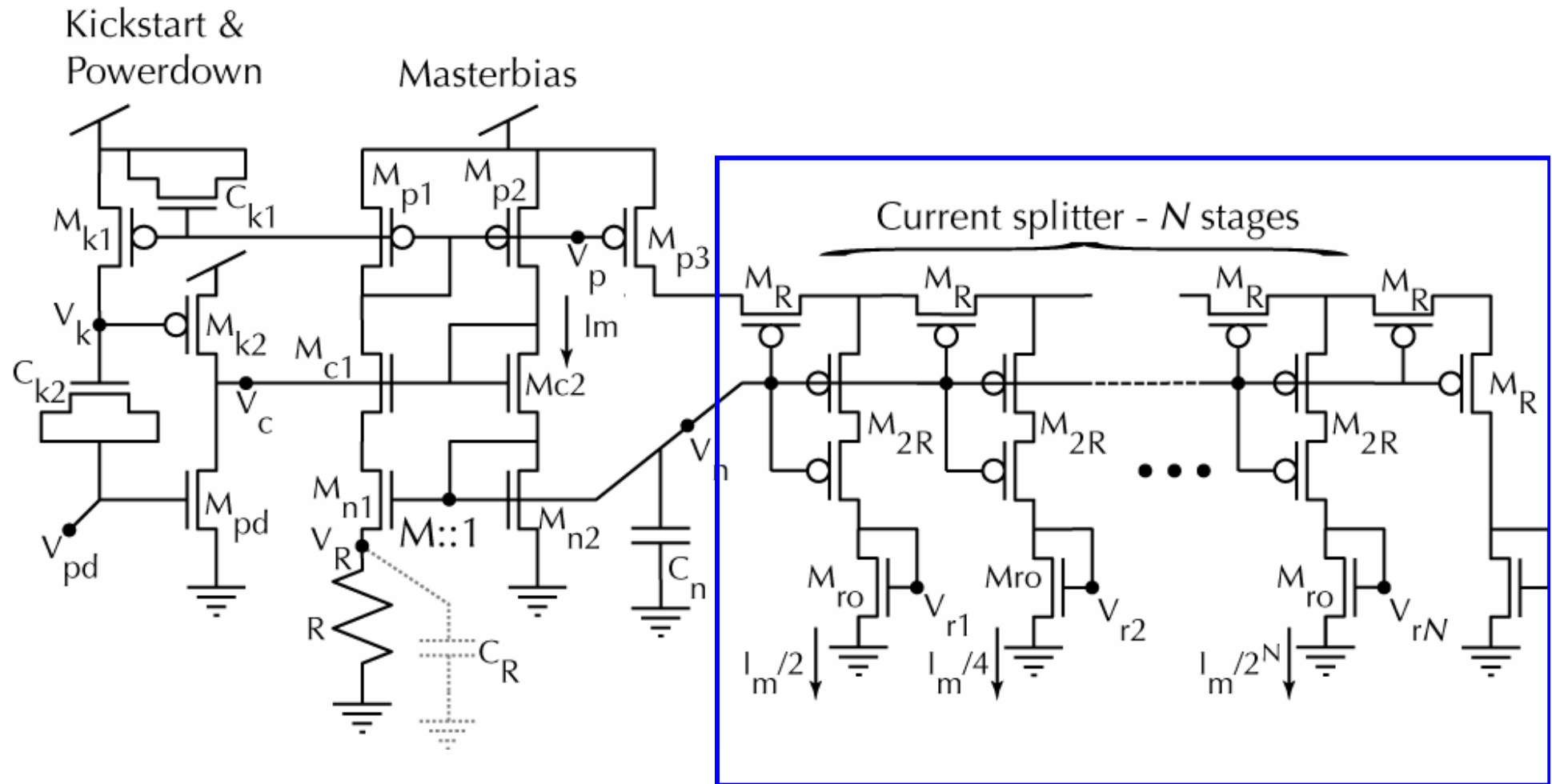

The current splitter



Klaas Bult was born in Marienberg, The Netherlands, on June 26, 1959. He received the M.S. degree in electrical engineering from the University of Twente, Enschede, The Netherlands, in 1984, on the subject of a design method for CMOS op amps. In 1988 he received the Ph.D. degree from the same university on the subject of analog CMOS square-law circuits.

He is now with Philips Research Laboratories, Eindhoven, The Netherlands. His main interests are in the field of analog CMOS integrated circuits.


Dr. Bult was a co-recipient of the Lewis Winner Award for outstanding conference paper of ISSCC 1990.



Govert J. G. M. Geelen was born in Heythuysen, The Netherlands, on November 20, 1957. He received the M.S. degree in electrical engineering from the University of Eindhoven, Eindhoven, The Netherlands, in 1983.

In 1984, after his military service, he joined the Philips Research Laboratories, Eindhoven, where he is currently engaged in the design of analog CMOS integrated circuits.

 Mr. Geelen was a co-recipient of the Lewis Winner Award for outstanding conference paper of ISSCC 1990.



Bult & Geelen
IEEE J. Solid State Circuits, 1992

Principle of current splitting


 


Fig. 1. The basic principle of current division.



I_{in} splits *only* according to geometry of transistors.

V_g , V_a , V_b , V_m , I_1 & I_2 don't matter!



Bias generator core circuit

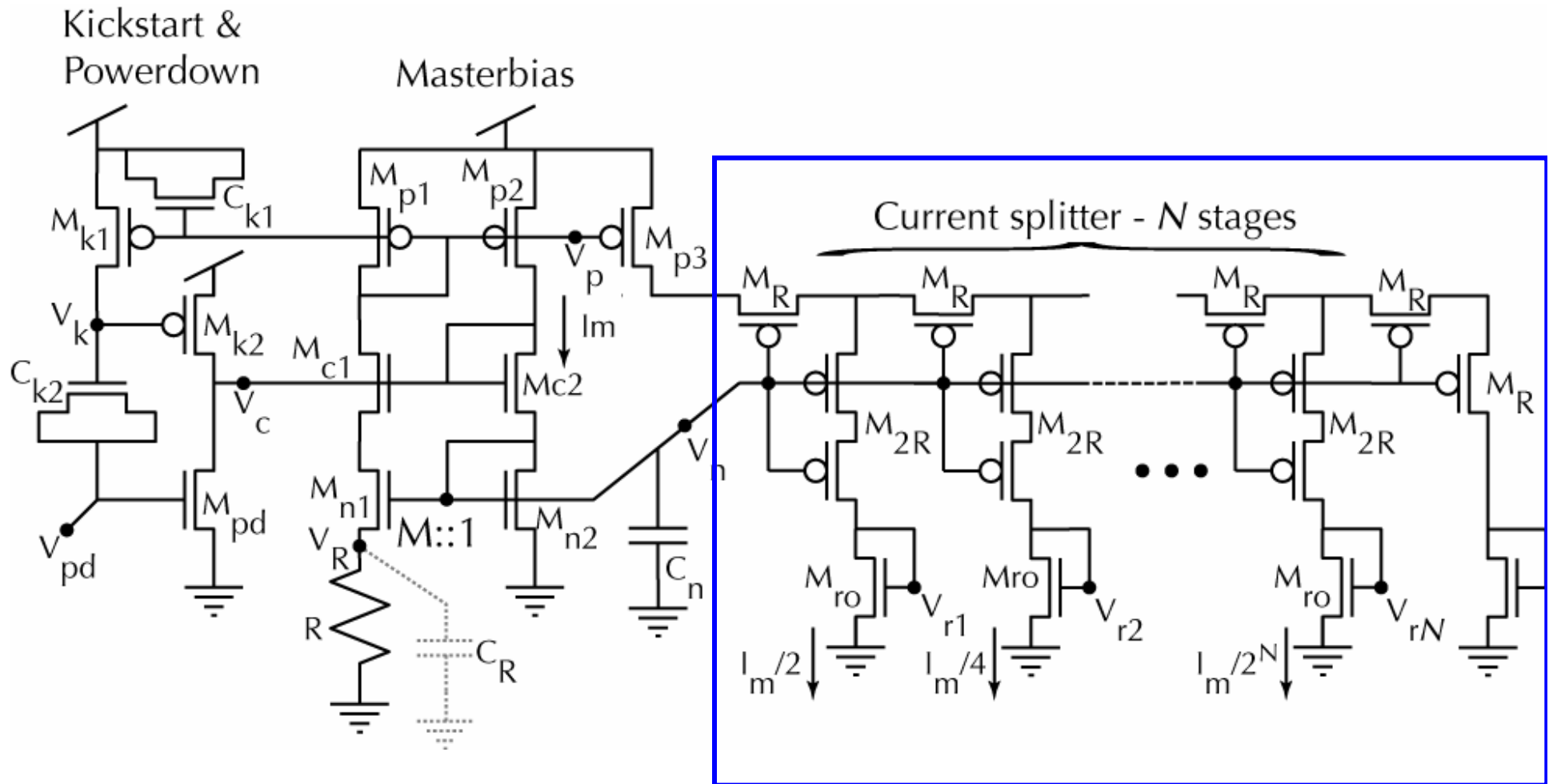

  
The splitter currents are accurate over at least 6 decades



  The generated currents are protected from effects of illumination



 
Copies of generated currents are useful down to a few I_0



To go even lower, use the fA current mirror from Linares-Barranco & Serrano-Gotarredona, JSSC 2003


Complete biasgen for chip

Masterbias

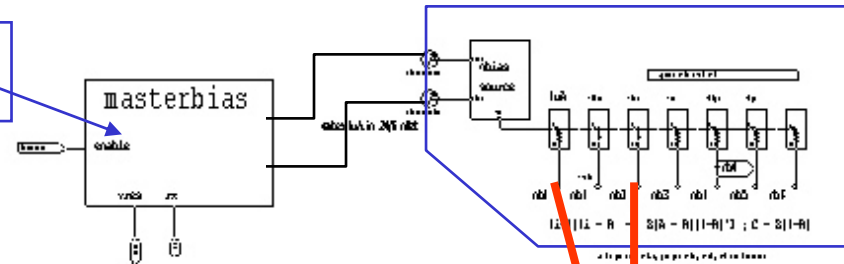


Current splitter


Biases

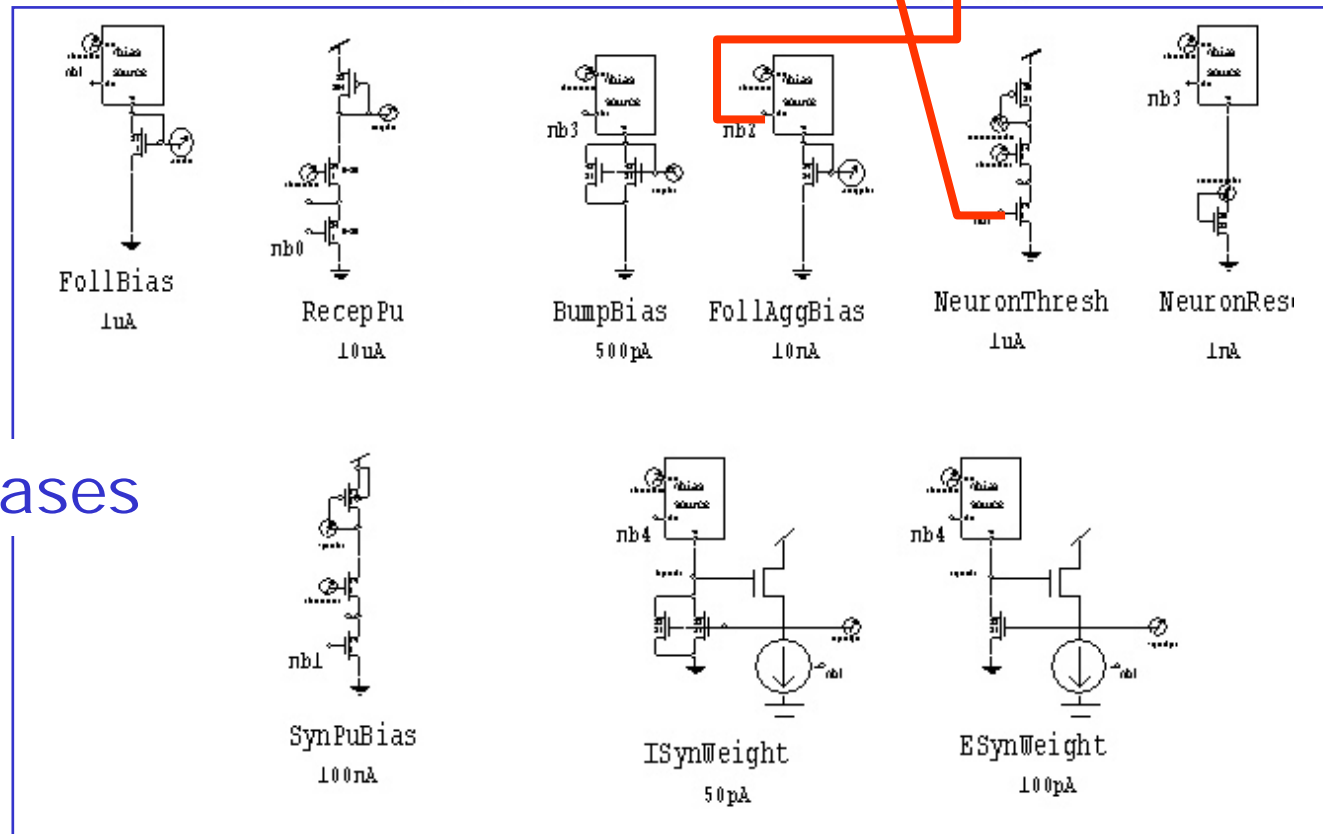



Bias current generator design kit

 

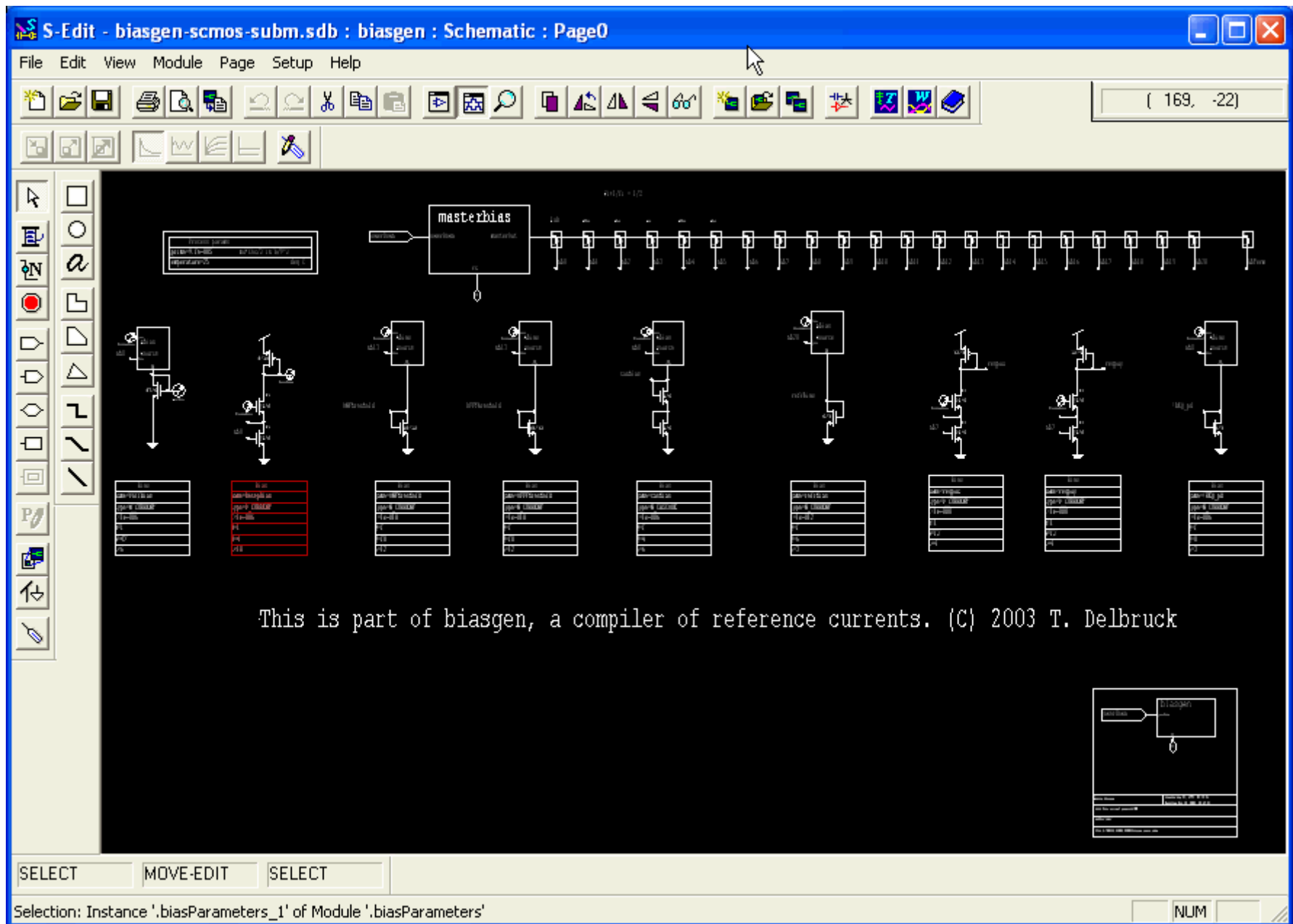- Compiles layout for a bias generator
- For Tanner tools (L-Edit, S-Edit, L-Comp) v.10+
- Layout uses MOSIS SCMOS scalable rules
- 2 metal, single poly
- Shielded from light and minority carrier diffusion



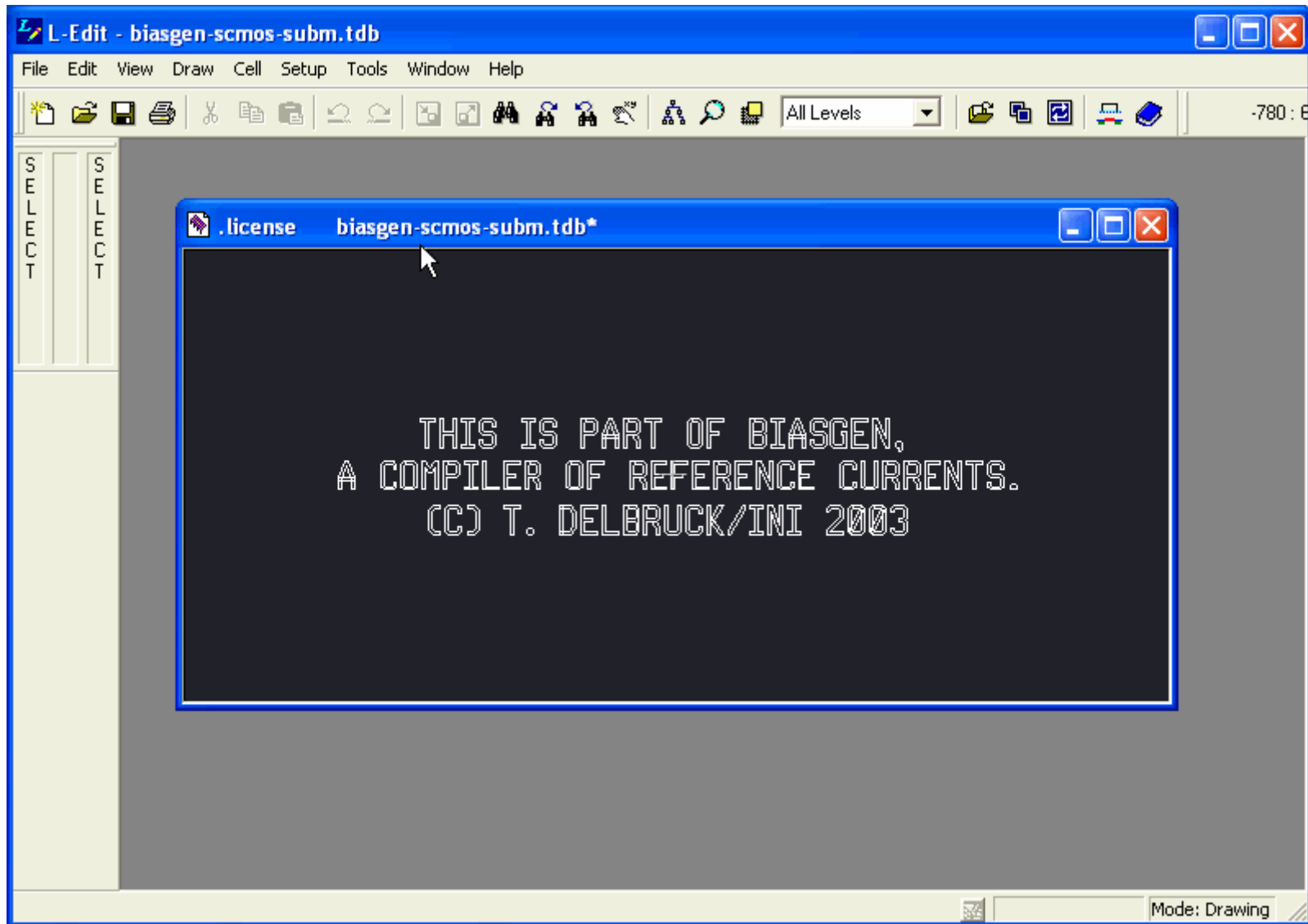

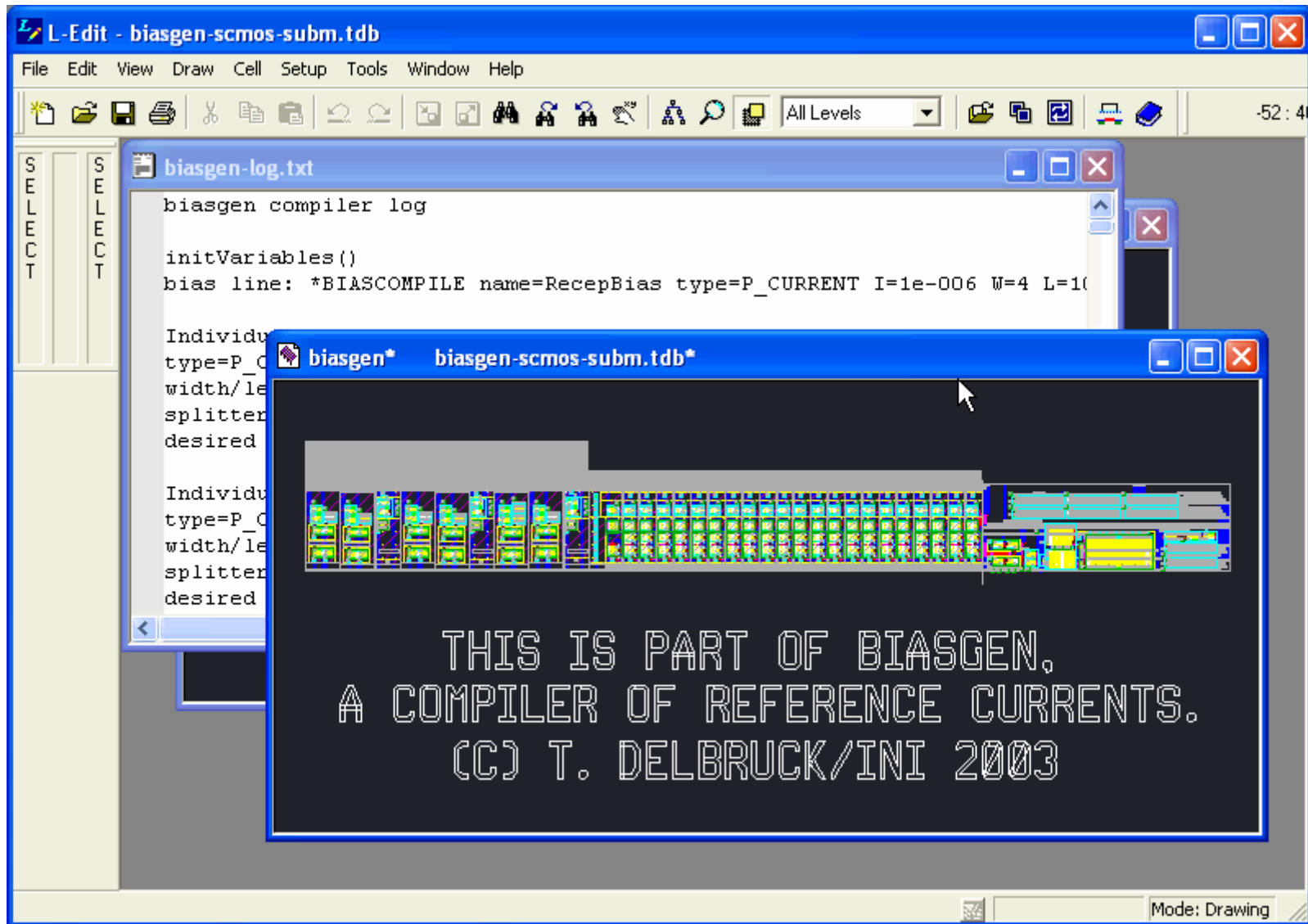

For more information, Google

Bias generator design kit

Future challenges

- Understand and control temperature effects
- Use Bernabe/Terressa trick to go to fA currents
- Develop good circuits to buffer bias voltages, so we don't need offchip bypass capacitors

Good luck!

- See <http://www.ini.unizh.ch/~tobi/biasgen>
- It has a bias generator design kit for MOSIS scalable processes that lets you build a bias generator very easily
- tobi@ini.phys.ethz.ch